

• Truth Table

Inputs		Output
A	B	Q
0	0	0
0	1	1
1	0	1
1	1	0

$2^n = \text{number of rows}$   
 $- n \text{ is \# inputs}$

$$A'B = Q$$

- Converting to equations

• Sum of Products (SOP)

- OR =  $A+B$      $A \mid B$      $A \vee B$

- AND =  $A \cdot B$      $A \& B$

- NOT =  $\bar{A}$      $A'$

OR gate - Run thru AND gate then OR gate

A	B	Q
0	0	0
$\bar{A}B$	0	1
$A\bar{B}$	1	0
$AB$	1	1

SOP

1. Invert inputs that are 0
2. Up/down a row  $\rightarrow$  ADD (OR)
3. Across a row  $\rightarrow$  MULTIPLY (AND)
4. Look where output = 1

$$\bar{A}B + A\bar{B} + AB = Q$$

If  $A=0$ ,  $01 + 0\bar{1} + 01$   
 If  $B=1$ ,  $11 + 00 + 01 = 1 + 0 + 0 = 1$

• Product of Sums (POS)

1. Look for output = 0
2. Across row  $\rightarrow$  OR (add)
3. Up/down row  $\rightarrow$  AND (multiply)
4. Invert inputs = 1

OR gate

A	B	Q
$A+B$	0	0
	0	1
	1	1
	1	1

$$A+B = Q$$

### AND Gate



$$Q = AB$$

$$Q = A \& B$$


### OR Gate



$$Q = A + B$$

$$Q = A | B$$

### XOR Gate

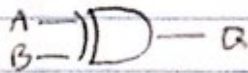

$$Q = A \oplus B$$

### NOT Gate



$$Q = \neg A$$


$$Q = A'$$

$$Q = \bar{A}$$

$$Q = \neg A$$

0 inverter bubble can be added to anything

- De Morgan's Law

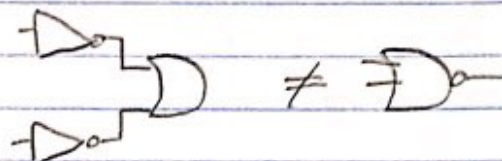

$$Q = (A + B)'$$

$$Q = (\bar{A} \cdot \bar{B})$$

• Can change OR's  $\rightarrow$  AND's, vice versa

- Where there's bubbles, remove

- Where no bubbles, add

NOT

$$Q = (A + B)' \Rightarrow Q = (\bar{A} \cdot \bar{B})$$

A	B	Q
0	0	1
0	1	0
1	0	0
1	1	0

A	B	Q
0	0	1
0	1	0
1	0	0
1	1	0


MAKE THIS

$$C = 0 \Rightarrow Q = A$$

USE SOP

A	B	C	Q
0	0	0	0
0	0	1	0
0	1	0	0 <sup>SOP</sup>
0	1	1	1 $\nwarrow$ <sup>SOP</sup>
1	0	0	1 $\nwarrow$ <sup>SOP</sup>
1	0	1	0
1	1	0	1 $\nwarrow$ <sup>SOP</sup>
1	1	1	1 $\nwarrow$ <sup>SOP</sup>


$$C = 1 \Rightarrow Q = B$$

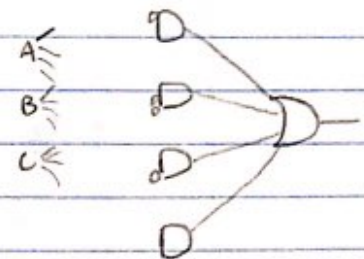

$$Q = \bar{A}BC + A\bar{B}C + AB\bar{C} + ABC \Rightarrow 4 \text{ AND's}$$




Cosc 130 (11/15)

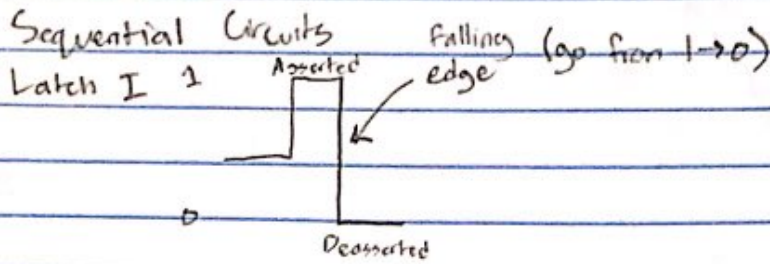

- If output is fed back as input, it's sequential

SR Latch Truth

S <sub>in</sub>	R <sub>in</sub>	Q
0	0	Q <sub>prev</sub>
0	1	0
1	0	1
1	1	0

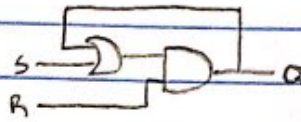

Sum Truth

Left	Right	S
0	0	0
0	1	1
1	0	1
1	1	0

Carry Truth

Left	Right	C
0	0	0
0	1	0
1	0	0
1	1	1

Data Latch (D-Latch)

(D)	(E)	Q
Data	Enable	
0	0	Q <sub>prev</sub>
0	1	0
1	0	Q <sub>prev</sub>
1	1	1

E=1, get D  
E=0, get Q<sub>prev</sub>

D-Flip-Flop (DFF)

Rising edge, falling edge

Finite State Machine

- Ex.: Lamp with L-M-H bulb (need 2 bits 0-3)

State L	State R	Switch	Q <sub>new L</sub>	Q <sub>new R</sub>
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	1	0
1	0	1	1	1
1	1	0	1	1
1	1	1	0	0

$$N_L = s(L_L \oplus L_R) + L_L s$$

$$N_R = L_R \oplus s$$